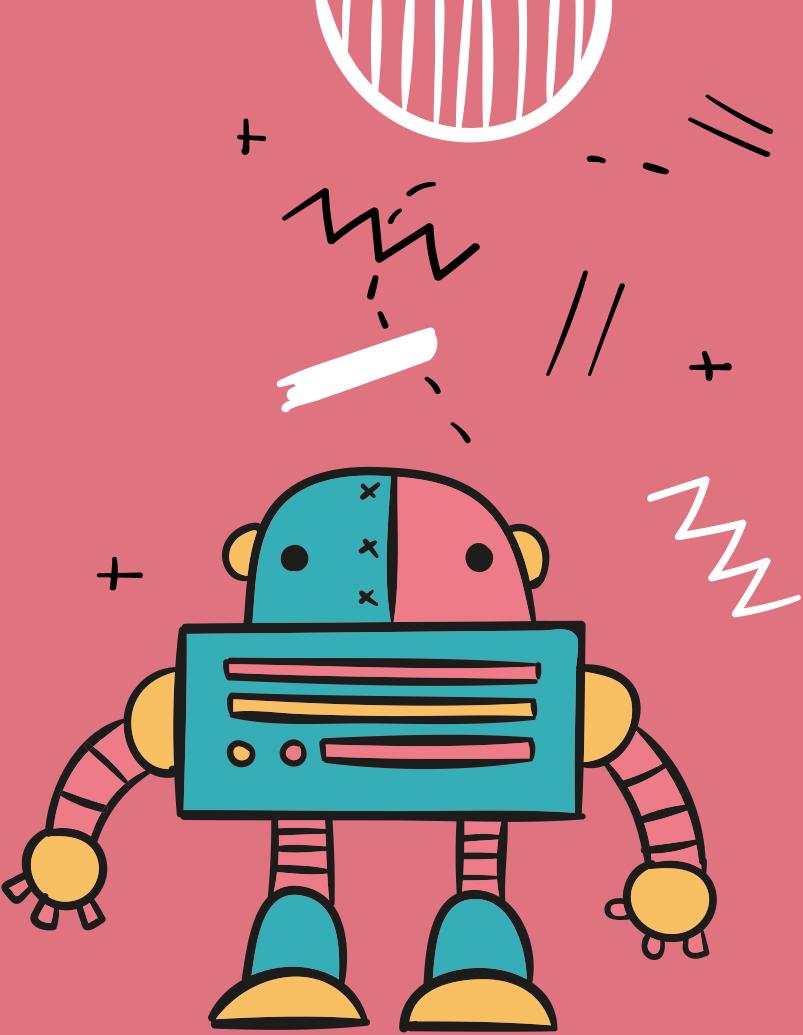






Electronics: from analog to digital

Gabriel Pedroza and Raphael Correia

Electrostatics





Electric charge: a fundamental property

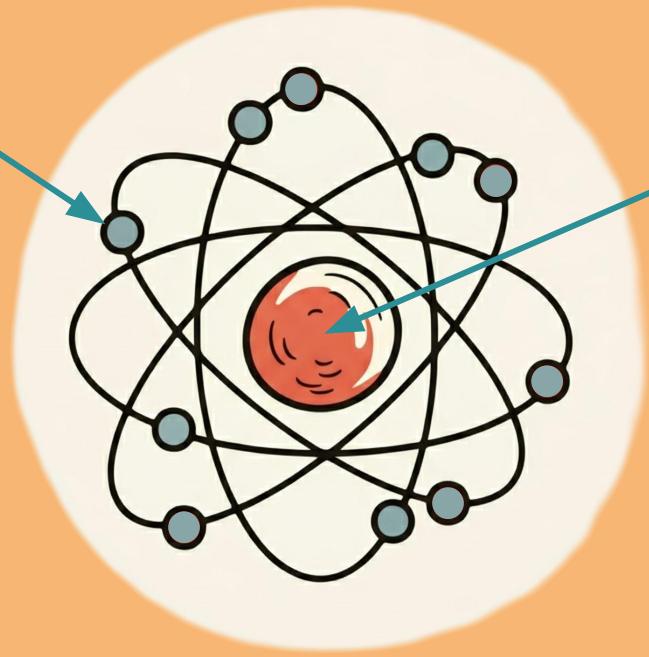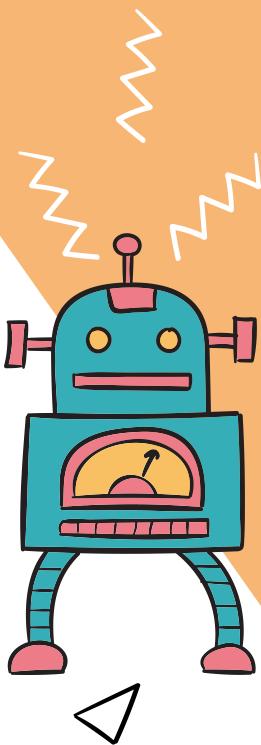

Proton +e

Electron -e

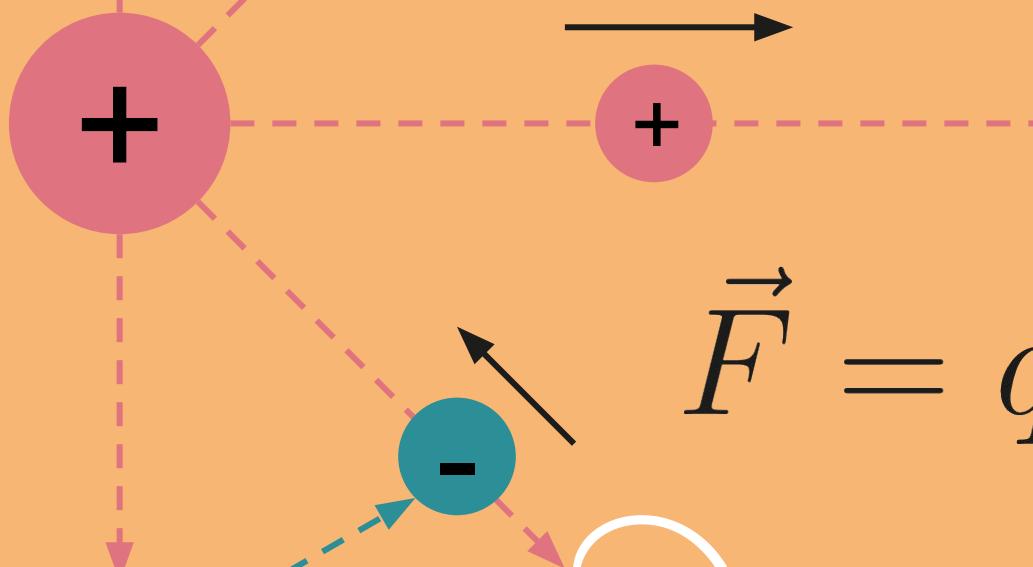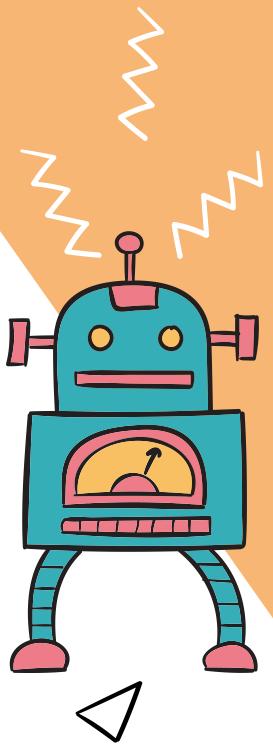
Electric charges make and suffer the effects of electric fields




$$\vec{F} = q \vec{E}$$

+

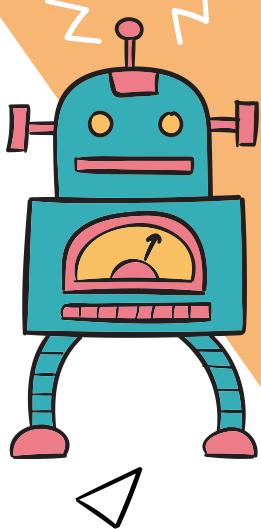
Walking along field lines changes potential energy



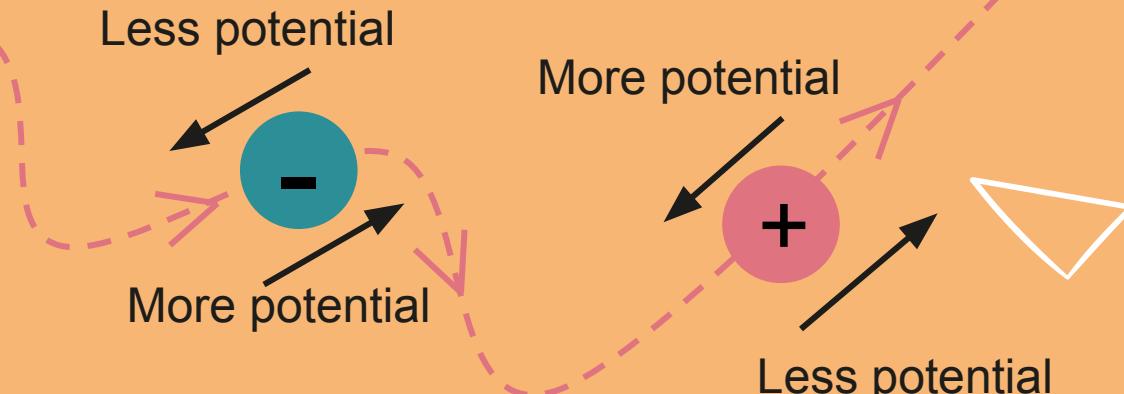→ General principle: charges move so that they have as *little* potential energy as possible




+

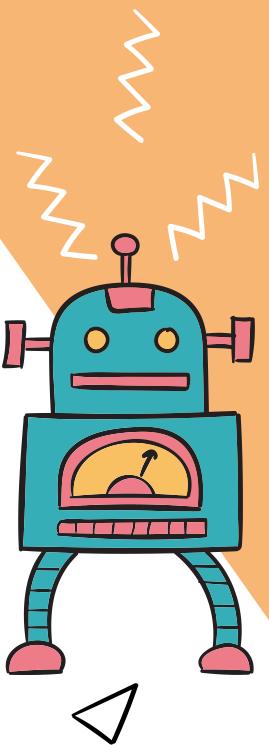



Voltage is all you need!

Due to mathematical reasons, we can define the voltage* at a point so that its spatial rate of change is the electric field ($E = dV/dx$)

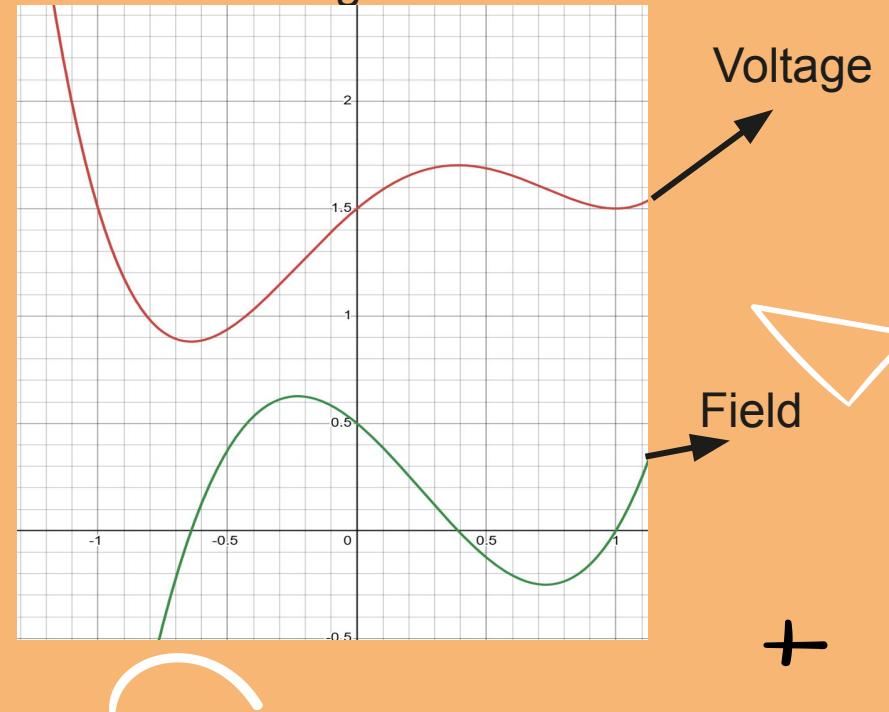Then, the potential energy of a charge is just $U = qV$



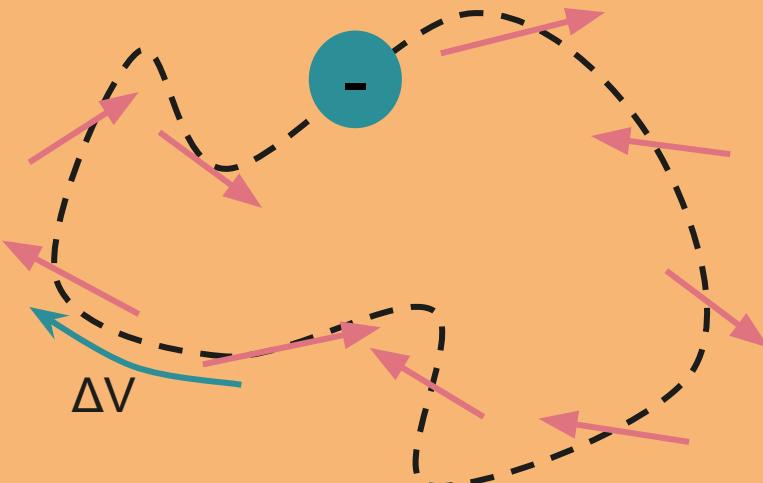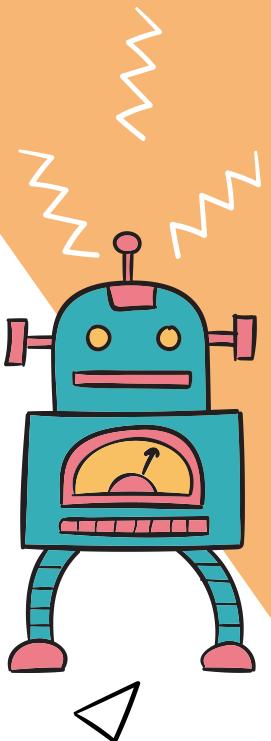Don't forget conservation of energy (kirchoff's voltage law)



Under nice* conditions, moving a charge along a cyclic path cannot change its potential energy. Thus:




→ The sum of all ΔV along a cyclic path is zero

*in practice, we can account for ugly conditions with further voltage differences

+


Don't forget conservation of charge (kirchoff's current law)

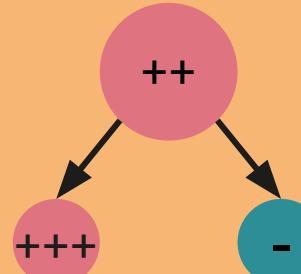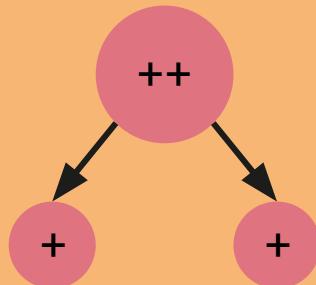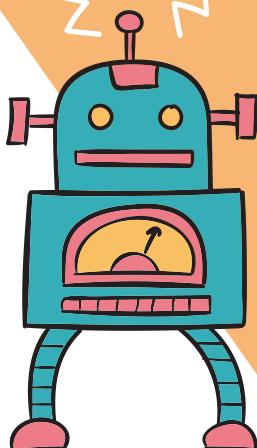
There is absolutely no way of making or destroying charge. All of it is always conserved.




+

Building circuits

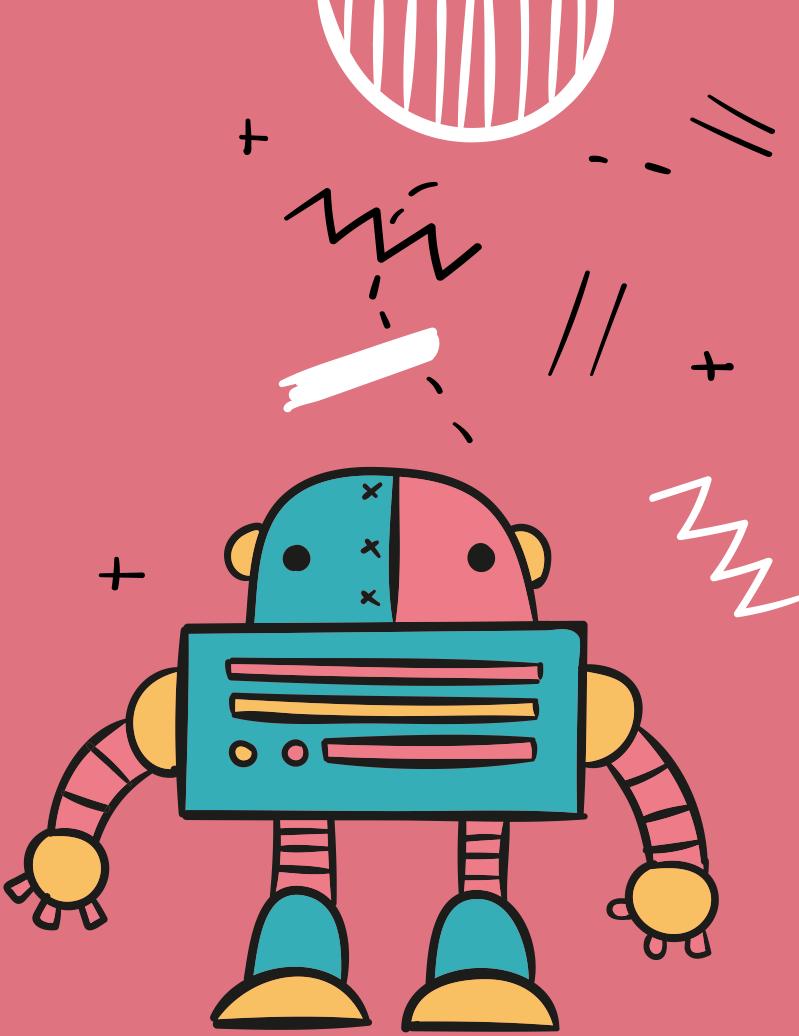

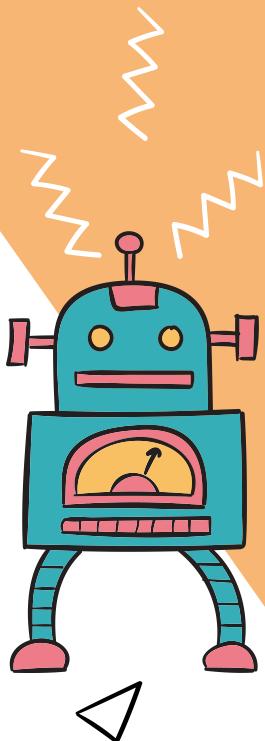

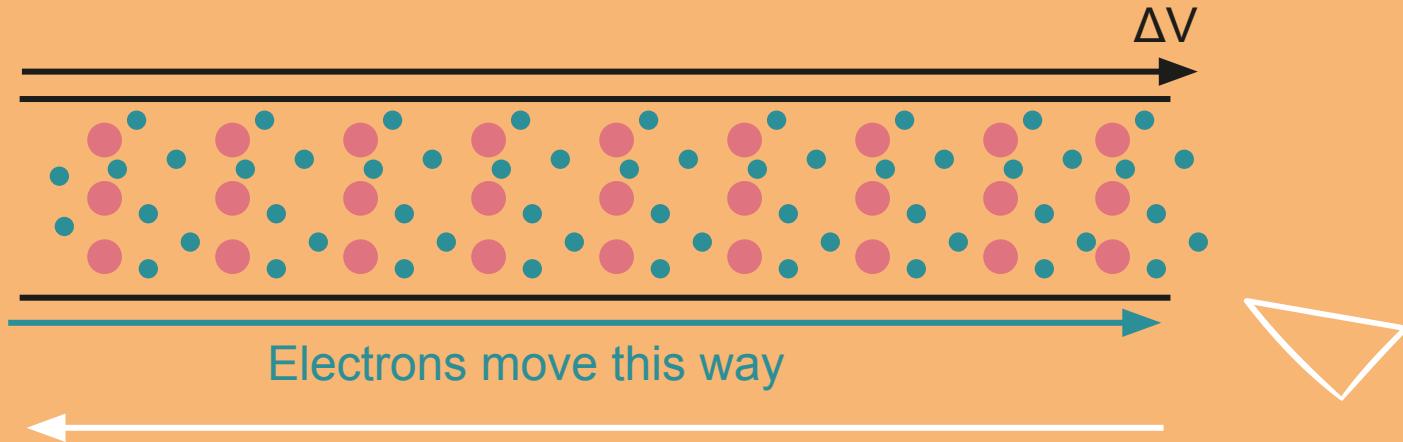Metals have a sea of free electrons available to move





We call the movement of charges *current*. In practice, we treat it as if there were positive charges moving in the opposite direction



+



Wires

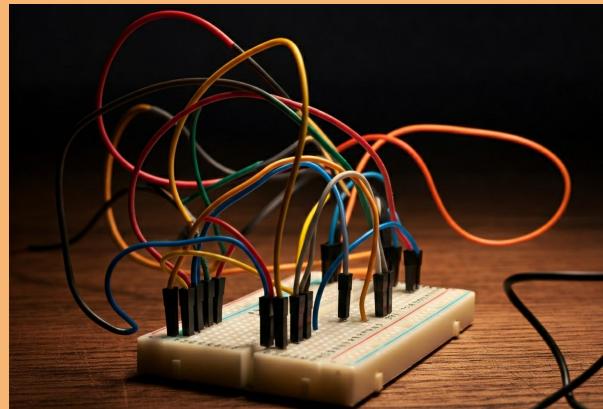
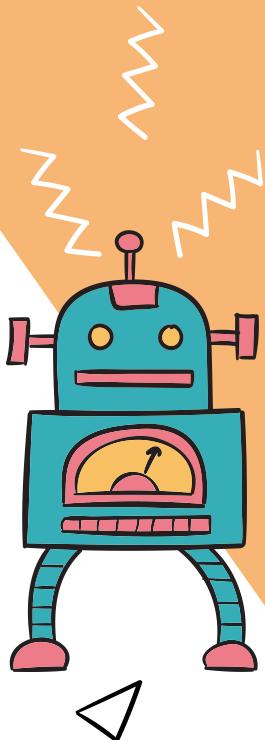
An (ideal) wire is a component that can conduct any amount of current without any voltage drop



Batteries and voltage sources

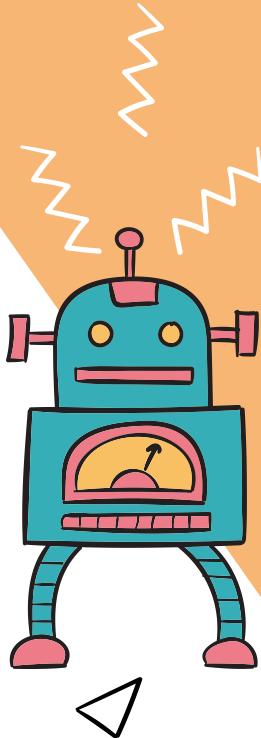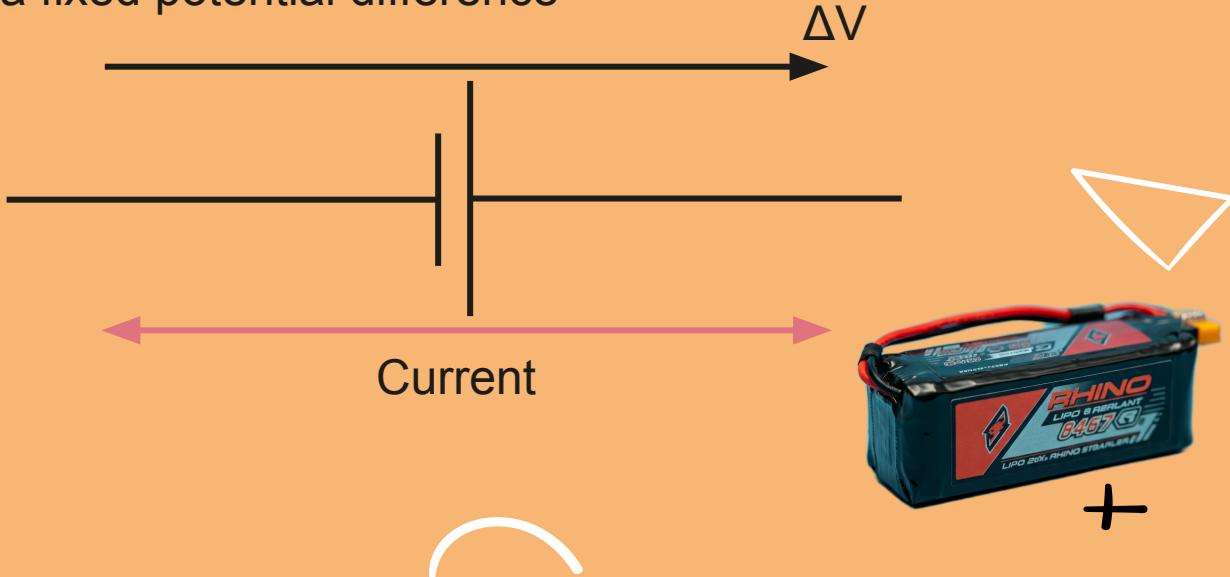
An (ideal) voltage source, or “battery”, is a component that can conduct any amount of current at a fixed potential difference





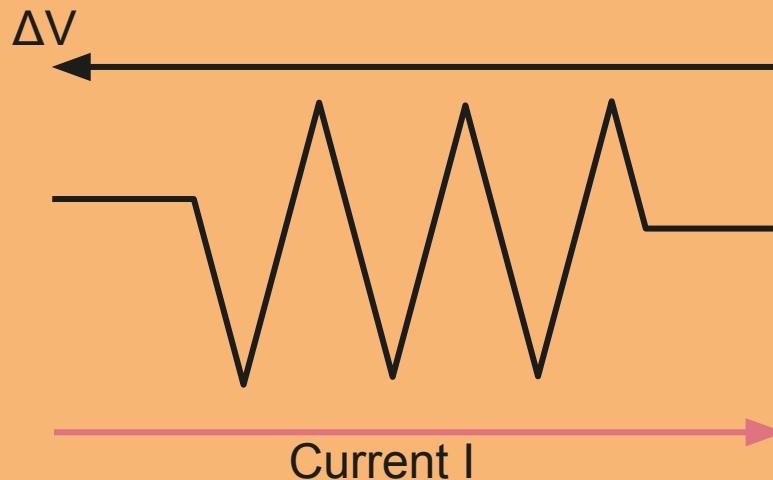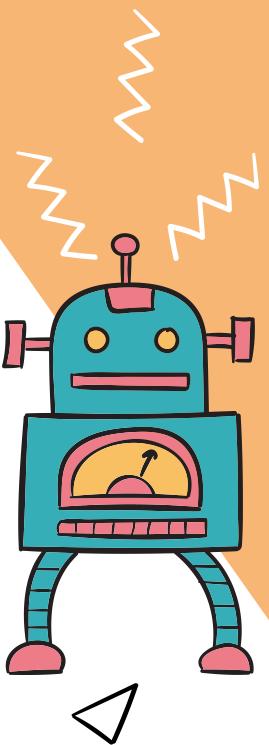

Ohm's law

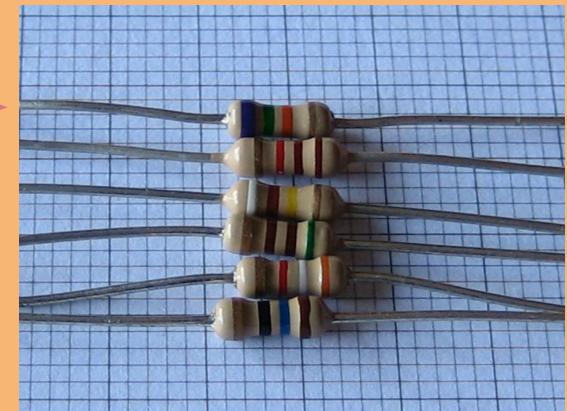An (ohmic) resistor is a component that obeys $\Delta V = RI$, for some constant R . We call R its resistance



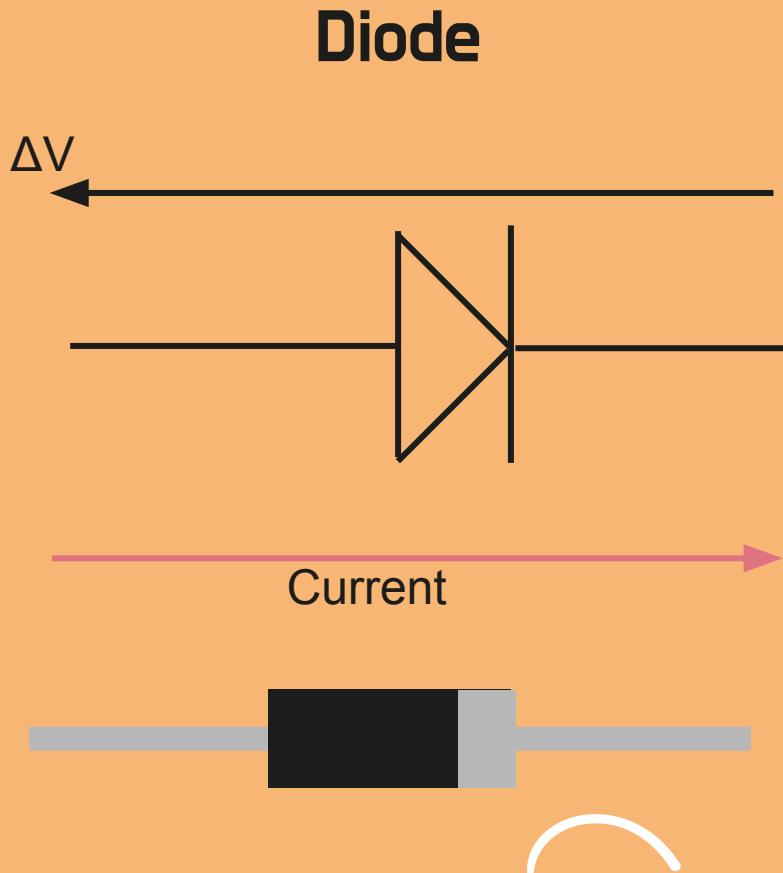
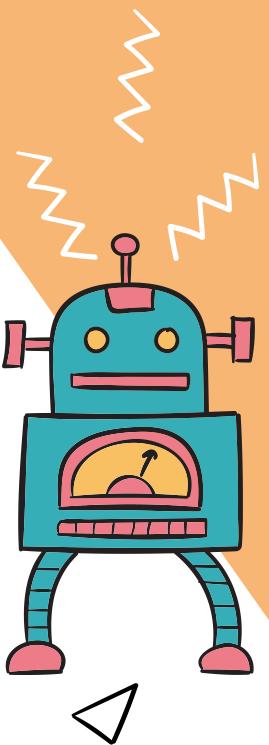


An (ideal) diode is a component that can conduct any amount of current, *in a single direction*, at a fixed voltage drop.

LEDs are diodes that emit light when current goes through them (longer leg is positive)


+

Using components to build circuits

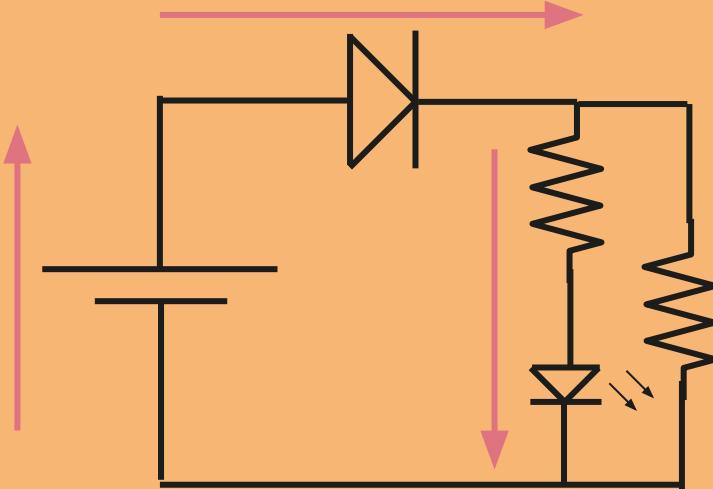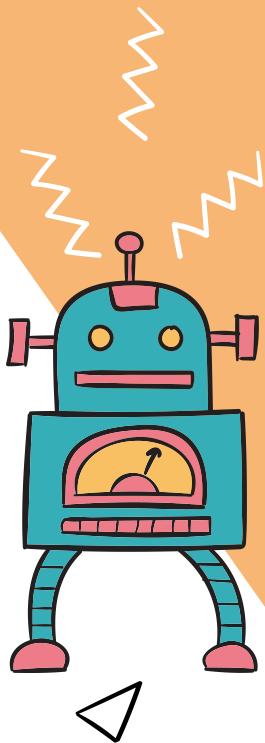

In practice, useful components have documents called *datasheets* that tell us how much voltage and current they need. Then we just need to wire a circuit capable of powering them.

Digital electronics and logic

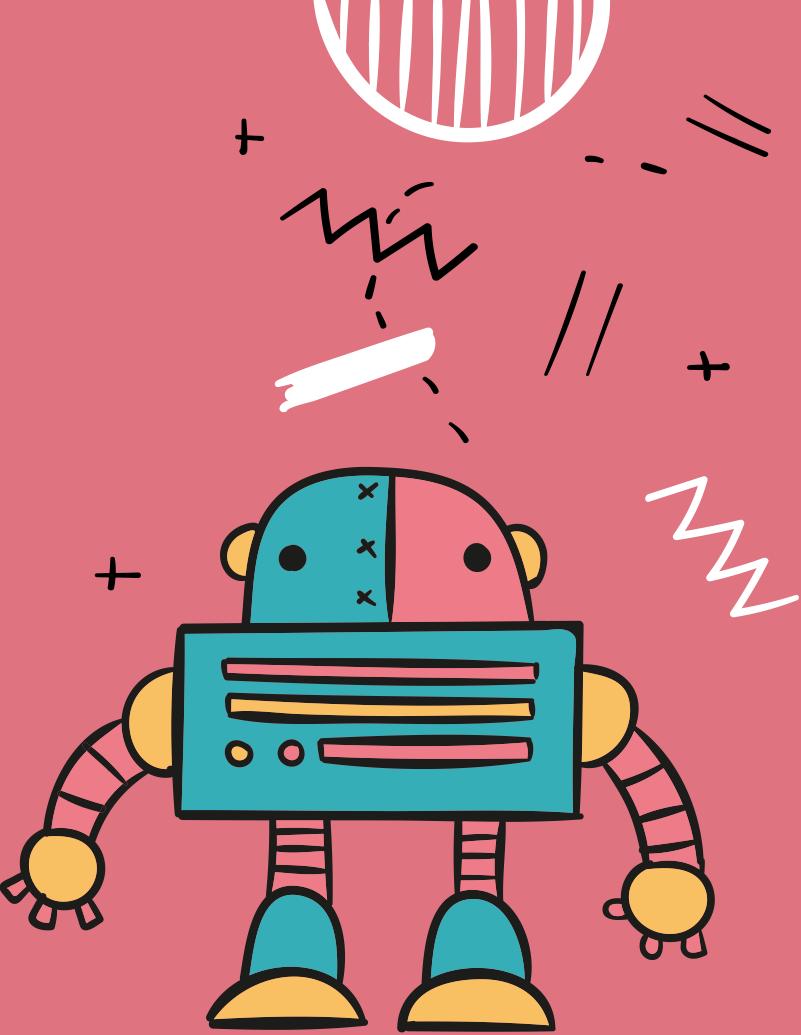


Digital electronics have two states

Very often, electronics operate just between two voltages: HIGH (e.g. 5V) and LOW (e.g. 0V). These are called digital electronics. We shall see some of them in the future, but the main one is the Arduino:



Boolean logic

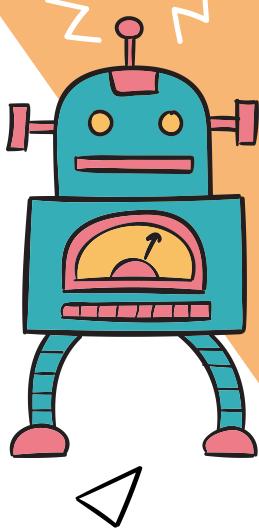We can abstract away HIGH and LOW voltages as 1 and 0 signals. Because they are ubiquitous across digital electronics, we need ways to combine multiple digital signals into a single one.




Furthermore, 1 and 0 can also represent truth values (e.g. $4 = 2 + 2$ is a statement which has value 1). Therefore, the power of combining signals is the power of combining the truth of multiple statements into a single truth value. This will be crucial when programming.

AND operator

Let x and y be two statements (or signals). Then the AND operator $\&\&$ is such that:

X	Y	X && Y
0	0	0
0	1	0
1	0	0
1	1	1

Both need
to be true

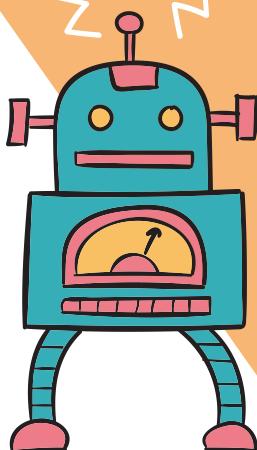

OR operator

Let x and y be two statements (or signals). Then the OR operator \parallel is such that:

X	Y	$X \parallel Y$
0	0	0
0	1	1
1	0	1
1	1	1

Either need
to be true

